



**FACULTATEA DE AUTOMATICĂ ȘI CALCULATOARE  
DEPARTAMENTUL CALCULATOARE**

**Digital Locker Cabinet**  
DSD PROJECT

Student: Măgerușan Alexandru-Ilie

Project supervisor: **Ileana Blaj**

**2025**

<b>1.Specifications .....</b>	<b>3</b>
<b>2.Design .....</b>	<b>4</b>
2.1 Black box .....	4
2.2Detail diagram.....	4
<b>3.Structure and functionality.....</b>	<b>5</b>
3.1 Functionality .....	Error! Bookmark not defined.
3.2 Resources .....	Error! Bookmark not defined.
<b>4.Utility and results .....</b>	<b>8</b>
<b>5.Further development .....</b>	<b>9</b>
<b>6.Technical justifications for the design .....</b>	<b>9</b>

# 1.Specifications

Encryption code application for security of cabinets

Description: Implement an application that allows the user to add a 3-digit cipher to secure a closet (similar to the lockers used in sports locker rooms, malls, etc.)

*Functional requirements:*

1. A FREE\_CONTRACTED LED will have the function of signaling that the cabinet is free (LED off) or busy (LED on)
2. The user will press an ADD\_DIGIT button to signal the start of entering the code. An INTRODU\_CHARACTERE LED will light to mark the status
3. The user will add 3 characters in a row using the UP and DOWN buttons
4. The characters are in the range 0-1 ... 8-9-A-B ... F
5. The current character is displayed on the SSD
6. To move to the next character, the user will press the ADD\_DIGIT button
7. The previous character entered remains displayed
8. The next character is visible on the display in the next position
9. After entering the third character, when you press the ADD\_DIGIT button, the SSD display will turn off and the encryption will be locked by turning on the FREE\_OCUPIED LED.
10. The ENTER\_CHARACTER LED will turn off
11. Existence of a RESET button / switch during the entry of the cipher to return to the initial state (the LIBER\_OCUPAT LED will go out, the SSD display is empty, the ENTER\_CHARACTERE LED will go out)
12. The user will press the ADD\_CYPTEP / switch button to start entering the code to unlock the cipher
13. Steps 2-8 will be repeated
14. When entering the last character, when pressing the ADD\_DIGIT button, the check will be made, if the entered code corresponds to the previous code.
15. In case of a tie, the FREE\_EN-occupied LED will light up, the ENTER\_Character LED will go out, the SSD display will go blank
16. In case of unevenness, the FREE\_EN-occupied LED will remain lit, the ENTER\_CARCATERE LED will go out, the SSD display will be empty.

*Example use case:*


The user chooses a closet with the Free\_occupied LED off. Press the ADD\_DIGIT button to enter the characters. The "0" character is visible on the SSD. Enter the first "2" character by pressing the DOWN button twice. On the SSD, the display changes with the push of a button, namely: 0-> 1-> 2. The user presses ADD\_DIGIT again to enter the second character "1". The user presses ADD\_DIGIT again to enter the second character "3". The user presses ADD DIGITAL again, the code is saved, the ssd content is empty, the FREE\_EN-occupied LED is on, the ENTER\_Character LED will go out.

## 2.Design

### 2.1 Black box



### 2.2 Detail diagram

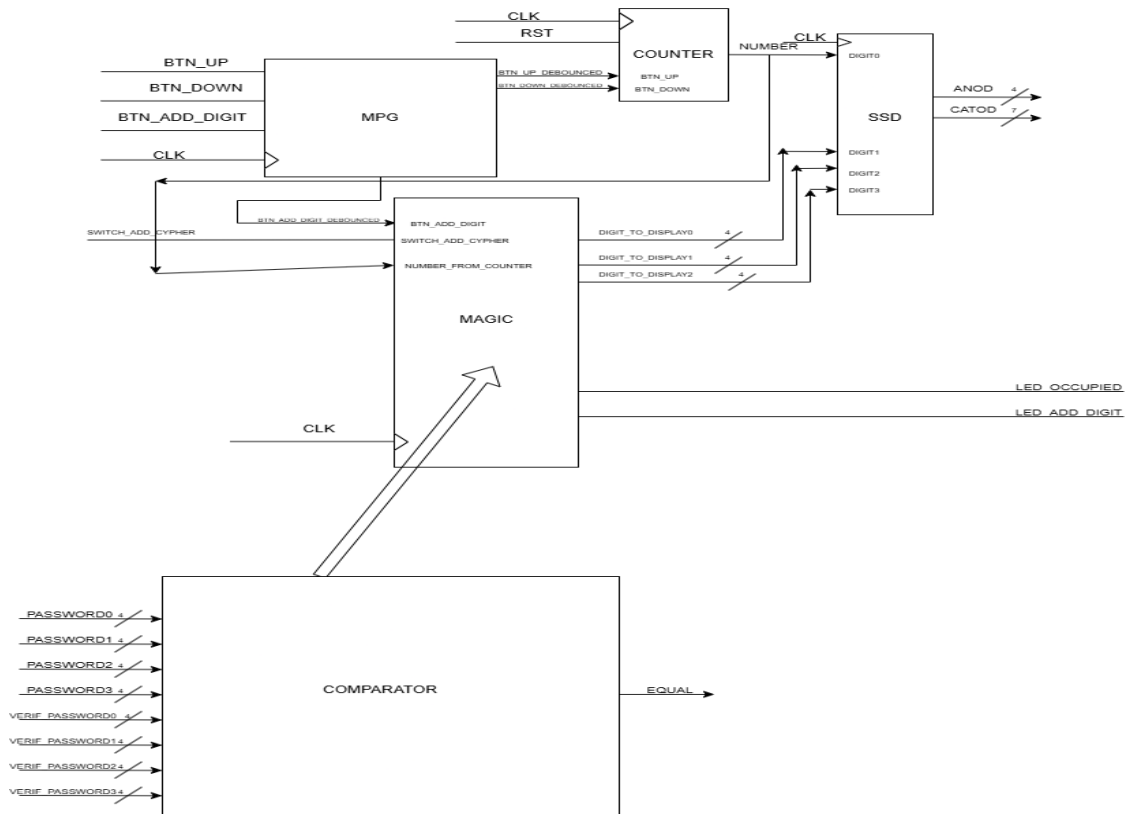


## 3. Structure and functionality

### 3.1 Functionality

Used components:


- MPG
- SSD
- COUNTER
- COMPARATOR
- ENCODER

MPG:

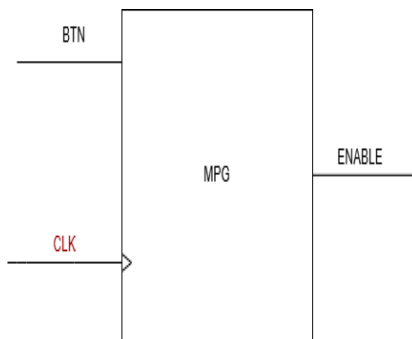


The „MPG” component fixes the way **BTN\_ADD\_DIGIT**, **BTN\_UP** and **BTN\_DOWN** work. When pressed, it makes sure each press counts as one input.

SSD:

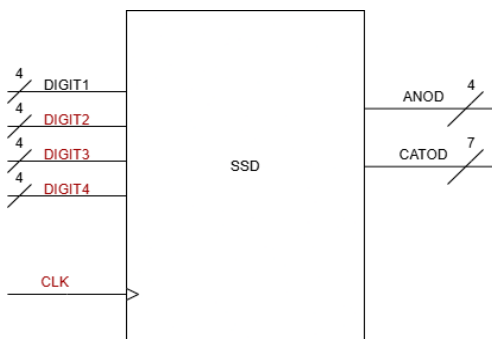


The **SSD** circuit turns 4-bit codes into signals that light up the correct segments of a 7-segment display.

## COUNTER:

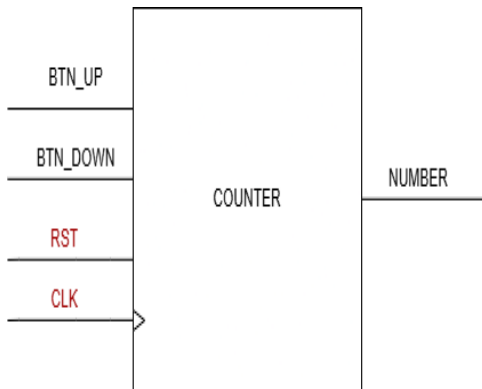


The **COUNTER** component can increase the number by pressing **BTN\_UP** or decrease by pressing **BTN\_DOWN**. The number ranges from (0 to F).

## COMPARATOR:

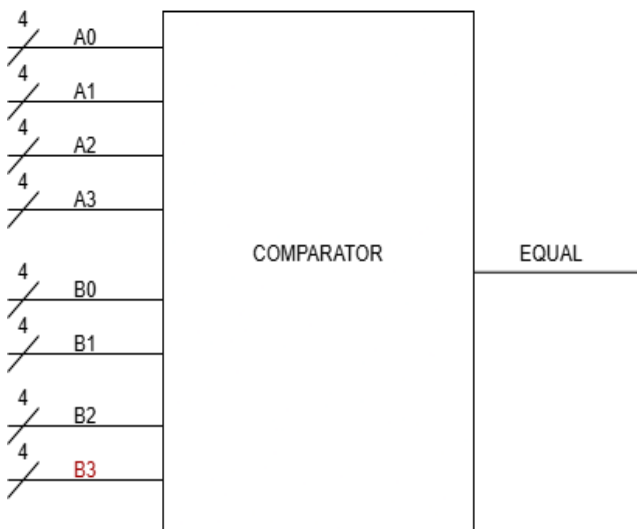


The **COMPARATOR** component checks if the 2 numbers are equal.

## ENCODER/MAGIC:

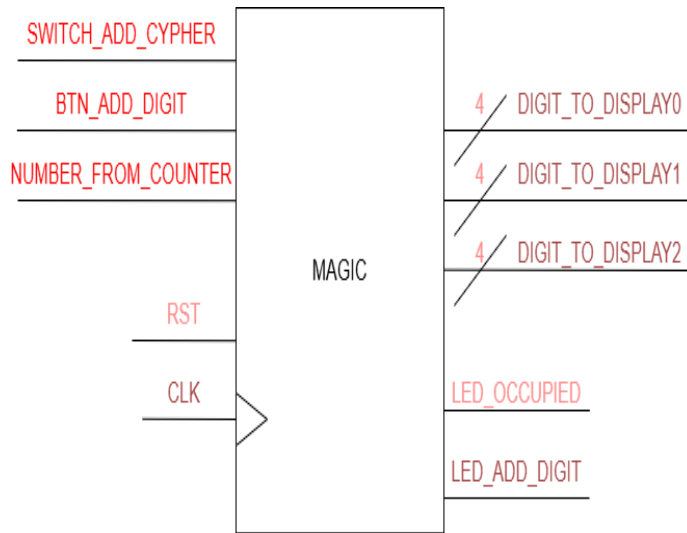

The **MAGIC** component stores the password and the verification code. Depending on them it changes the state of the **LOCKER** from **LED\_OCCUPIED** **ON/OFF**. It always

Flowchart:

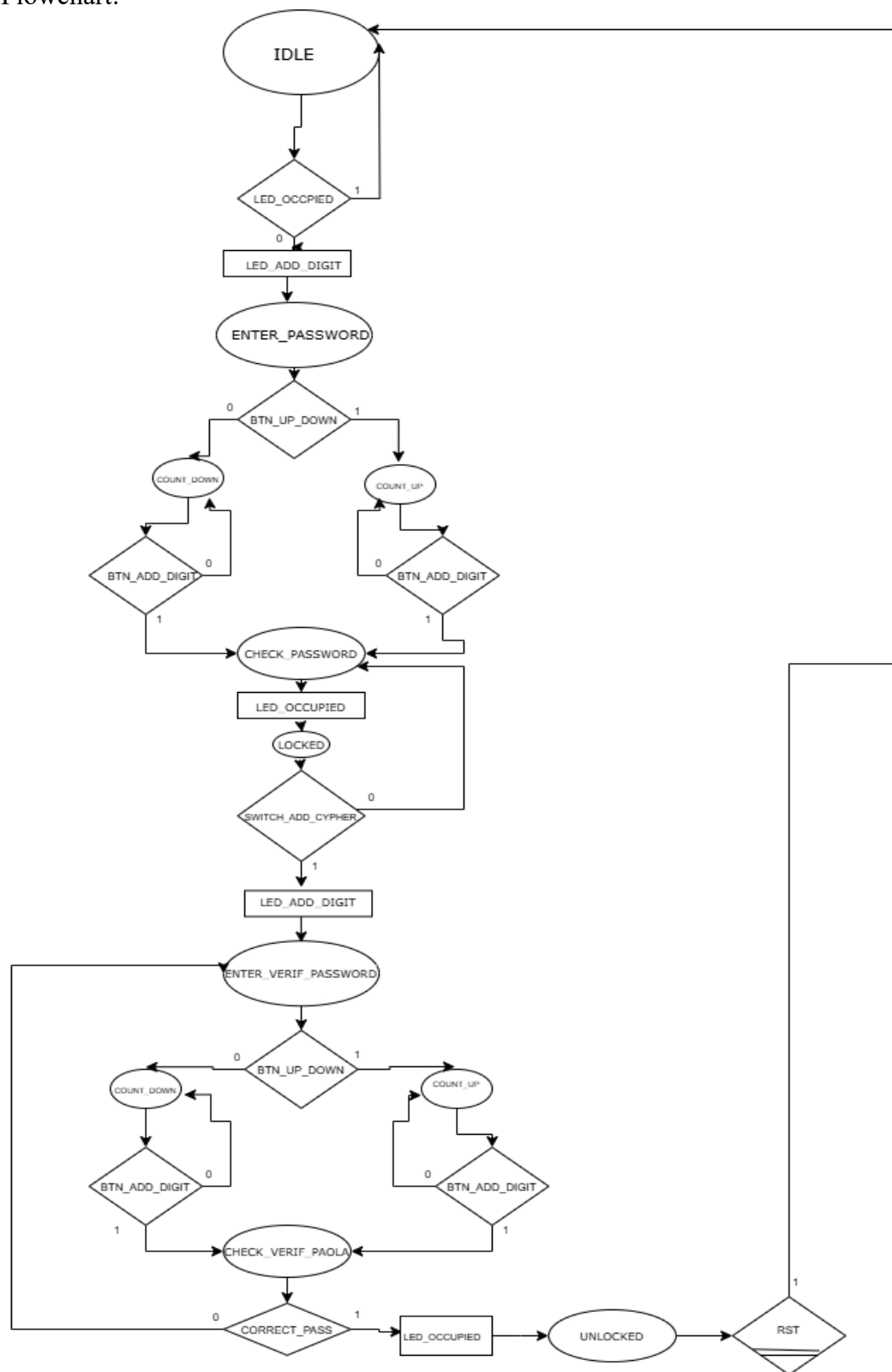



## **4.Utility and results**

**Utility:** Secure, reusable locker system with low power consumption.

**Results:** Successful encryption/decryption of 3-digit codes. Clear visual feedback via LEDs and SSD.

## **5.Further development**

- Add biometric authentication (fingerprint).
- Implement Wi-Fi connectivity for remote monitoring.
- Expand character set (e.g., symbols) for stronger security.

## **6.Technical justifications for the design**

- Simple Interface: Buttons + LEDs ensure user-friendliness.
- Modular Components: Easy maintenance/upgrades (e.g., swap SSD for LCD).
- Efficiency: Minimalist design reduces cost and complexity.